


## Fall 2024 VLSI Design/CAD VLSI Design

### Homework Assignment 1

Due date: Oct 11 Friday

 **Problem 1. Using Verilog to design and test an arithmetic logic unit (ALU).**

**ALU Module Design:** This ALU has three inputs, two 32-bit signed inputs, one 3-bit ALUOp input, and one 32-bit signed output.



**Testbench Design:** The test results should be printed on the screen with format as below (for example):

“1<sup>st</sup> Test data: input A is 1, input B is 2, ALUOp is 010, result is 3.”

“2nd Test data: input A is 3, input B is 4, ALUOp is 110, result is -1.”

...

**Note:** All the five functions of ALU need to be tested.

**Materials to be submitted:**

1. Verilog codes for ALU module
2. Verilog codes for testbench
3. Image of the screen that shows the test results.